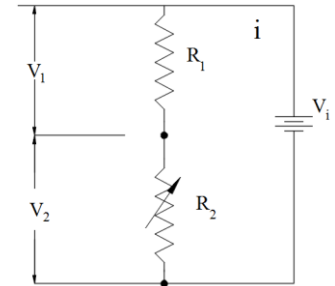



1-Use the Circuit Wizard-student edition version software to sketch the voltage divider circuit. Prepare a table for your results as shown below. For  $V_i=9\text{ V}$ ,  $R_1=900\ \Omega$ , and  $R_2$  of your choice between 100 and 5000  $\Omega$ . Calculate manually the current  $i$ ,  $V_1$  and  $V_2$ .

Case	$V_i$	$R_1$	$R_2\ (\Omega)$	$i$	$V_1$	$V_2$
1	9	900				
2	9	900				
3	9	900				
4	9	900				




2-Sktech the Wheatstone bridge circuit on circuit wizard. Prepare a table and find the output voltage  $E_o$  in each case. Select  $R_3$  to be between 50 and 200  $\Omega$ , and fill the table below

Case	$R_1$	$R_2$	$R_3$	$R_4$	$E_i\ (V)$	$E_o$
1	120	120		120	5	
2	120	120		120	5	
3	120	120		120	5	
4	120	120		120	5	

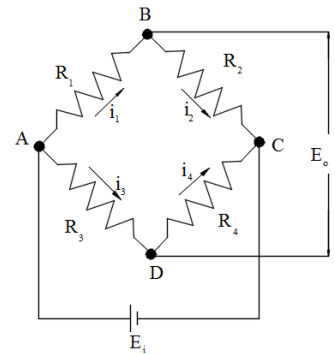

3-Sktech a circuit for inverting OP-AM (Inverting Operational Amplifier) and complete the following table of your choices. What do you conclude?


Case	$R$	$R_f$	$V_i$	$V_o\ (V)$
1				-5
2				-15
3				-2
4				-0.5

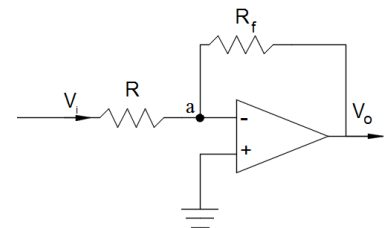

4- Create an RC time circuit as shown. Complete the table below of your choices

Case	$V_i$	$R_1$	$C_1$	time constant ( $\tau=RC$ )
1				0.1 s
2				1 s
3				10 s

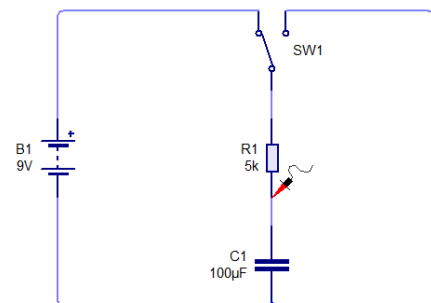Attach the variation of capacitor voltage with time for the case of charging and discharging the capacitor, with  $\tau=17$  seconds



5-By searching the internet and using Circuit Wizard construct a simple circuit using one or two transistors. Explain how the circuit works, and where the circuit is used practically.